

Description of the project:

Design an amplifier with the below specifications:

- 1) only **BJT** transistors can be used.
- 2) $V_A = 100\text{ V}$, $|V_{CE-sat}| = 0.2\text{ V}$, $|V_{BE-on}| = 0.7\text{ V}$
- 3) it should be a differential amplifier with two inputs and one output.
- 4) $V_{CC} = -V_{EE} = 5\text{ V}$
- 5) $A_{v-diff} \geq 40,000$
- 6) $Output\ Swing \geq \mp 3.5\text{ V}$
- 7) $I_{c\ min-transistors} = 50\ \mu A$
- 8) you can not use current source and you have to design it if you want a current source.
- 9) minimize the consumption of power.
- 10) calculate CMRR of your amplifier.